






XPerts in Power - Module 4


Harmonics


Diana Izvorska




Module Content


- What is a harmonic?
- Power supply harmonic distortion
- Why is power supply harmonic distortion a problem?
- Legislation
- Solutions in power supplies
 - Passive power factor correction
 - Active power factor correction
- Advantages and disadvantages
- Real and apparent power & efficiency
- A practical look at harmonic distortion & power factor





What is a Harmonic

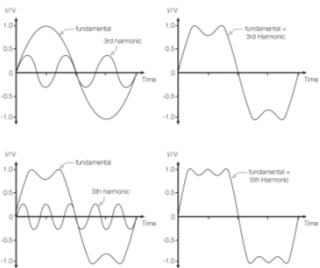



Power supply harmonic distortion

Better power factor = Lower harmonics because waveforms are cleaner

XP Power

Power Supply Harmonic Distortion

XP Power

Why is Harmonic Distortion a Problem ?

- Need to supply apparent power
- Ability to charge for apparent power
- Mains voltage distortion
- Over-sizing of power conductors
- Overheating Neutral conductors

FIGURE 16
Waveforms illustrating the peak flattening effect that the narrow current pulses impose on the mains voltage.


XP Power

Legislation


• EN61000-3-2

Only applies in Europe
 Measured at 230Vac
 Harmonic current distortion by harmonic up to 40
 AC supplies up to 16A per phase
 Class A - All equipment not in B,C or D
 Class B - Portable tools
 Class C - Lighting
 Class D - PC's, PC monitors & colour TV

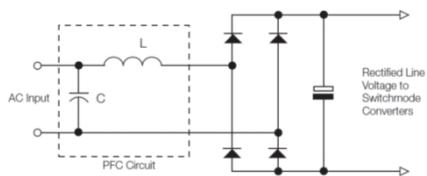Power Factor Correction in PSUs - Passive



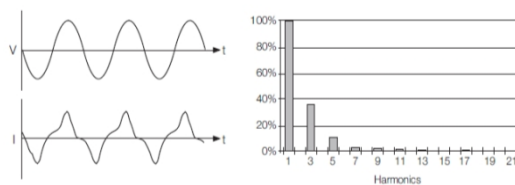
Power Factor Correction in PSUs - Passive





Passive PFC Advantages & Disadvantages

Advantages	Disadvantages
Simple	Heavy & bulky components (50Hz)
Cost effective	AC range switching required
Reliable & rugged	Low Power Factor (high input current)
No noise (EMI)	Cannot use multiple power supplies
Assists filtering	


 XP Power 10


Power Factor Correction in PSUs - Active

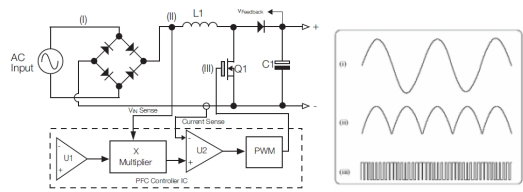

 XP Power 11

Power Factor Correction in PSUs - Active

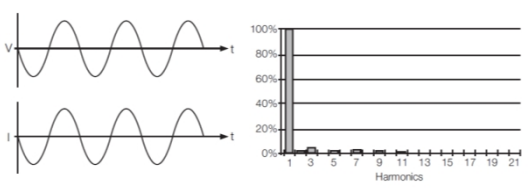

 XP Power 12

Active PFC Advantages & Disadvantages

<p>Advantages</p> <ul style="list-style-type: none"> current Universal High Power factor >0.9 Low input current Regulated high voltage bus Hold-up time EN61000-4-11 Multiple power stages 	<p>Disadvantages</p> <ul style="list-style-type: none"> High cost High complexity High component count Lower MTBF (calculated)
--	---

XP Power 13

Real & Apparent Power and Efficiency

Power (W) = Voltage (V) x Current (I)

- Real power is the useful power into the converter & must be used for efficiency calculations
- Apparent power is the power the mains must supply to the converter
- Power factor is a measure of the amount of useful power that is being drawn from the mains supply

Power (W) = Apparent Power (VA) x Power Factor (PF)

XP Power 14

Real & Apparent Power and Efficiency

Eff (%) = (output power (W) / input power (W)) x 100

Input power = Input voltage x Input current x PF

Output power = Output voltage x Output current

XP Power 15

16

18

