














XPerts in Power – Module 5
Real & Apparent Power
 Les Chant



2

What is Power?

- Power is the rate at which work is done
- In an electrical system, the more power in the system the more electrical work can be done (over a set period of time)
 - Power (W) = Work (J) / Time (seconds) or
 - Work (J) = Power (W) * Time (seconds)
 - Power (W) = Volts (V) * Amps (A)
 - I.e. you have more power when you have electrons pushing with more force (higher voltage) and also when you have more of them per period of time (higher current).






3

Real, Reactive and Apparent Power

- This is defined as the active power dissipated into the load – i.e. the useful power.
- Real, Reactive and Apparent power is symbolised by P and is measured in Watts (W)

Real Power

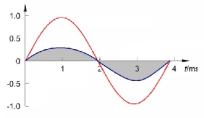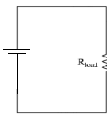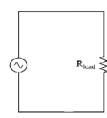XP Power

4

Reactive Power

- Reactive power is stored in the load and then returned to the source - it is not dissipated
- It is symbolised by the letter Q and measured as Volts-Amps-Reactive (VAR)

XP Power

5

Apparent Power


- Total power in a circuit, both dissipated and reactive is referred to as apparent power
- It is symbolised by the letter S and is measured in Volt-Amps (VA)

XP Power

6

Three Types Of Power

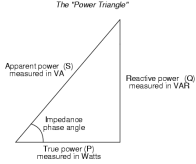- Trigonometrically related to each other.
- In a right angled triangle
 - P (real) is adjacent length
 - Q (Reactive) is opposite length
 - S (Apparent) is hypotenuse length
- The opposite angle is equal to the impedance of the circuit - The Cosine of this impedance gives the "Power Factor"



The "Power Triangle"

Apparent power (S) measured in VA

Reactive power (Q) measured in VARs

Impedance phase angle

True power (P) measured in Watts

XP Power

7

What is Power Factor?


- Power Factor is a characteristic of AC circuits
- Always a number between 0 and 1: the closer to 1, the better the power factor
- Power Factor = Real Power/Apparent Power
- Practical equations are;
 - $VA = W/PF$
 - $W = VA \cdot PF$
- The Power Factor is affected by Phase Shift & Harmonics

XP Power

8

Inductive Loads

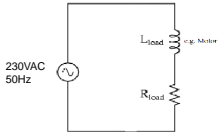- Here is a simple circuit showing an inductive load
- In real components there is also a resistive component to the load hence R load is shown



230VAC 50Hz

L_{load} c.g. Motor

R_{load}

XP Power

9

Out Of Phase Current and Voltage - Motor Load

- Application with inductive load (motor)
- Here we can see that the current is lagging behind the voltage by a certain angle
- The Grey area shows "Real Power" and the green shows "Reactive power"
- This angle represents the phase shift - this directly relates to the PF

XP Power 10

Phasor Angle Real and Reactive (Apparent)

- Here the load shows an inductive characteristic
- It is said to be lagging by phase angle Theta (θ)
- The apparent power exceeds the Active power
- CIVIL – capacitive current before voltage, inductive current after voltage

XP Power 11

Efficiency of Power Transfer

- Runner analogy

Cosine α (30°) = 0.87
or Power Factor = 0.87
or Efficiency = 87%


In other words, only 87% of the energy burned is being used to move the runner in the horizontal direction of A, and so extra energy will be required to achieve the same objective.


XP Power 12

Resistive Loads

- This shows a simple lamp load circuit
- There is no reactive (capacitive or inductive) component
- The lamp represents a simple resistive load


230VAC
50Hz

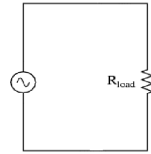



13

In Phase Voltage and Current - Lamp Load

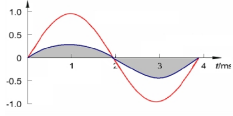
- Typical application resistive load like a light bulb
- There is no phase shift between the voltage and the current
- The grey indicates real power being delivered
- Therefore $\cos \phi = 1$
- PF = 1




14

Efficiency of Power Transfer


- Runner analogy



When the running surface is flat, then angle ϕ is zero degrees (0°)

$\cosine \phi (0^\circ) = 1.00$
or Power Factor = 1.00
or Efficiency = 100%

In other words, 100% of the energy burned is being used to move the runner from A to B.


15

Phase Angle Correction (Addition of Capacitive Component)

- When a capacitive element is added the apparent and real powers are brought closer together.
- This is seen typically in Power Factor corrected loads
- An inductive element would need to be added if the apparent power were to be leading the real power.

XP Power 16

What is a Harmonic

Any waveform that is not sinusoidal has a harmonic content

XP Power 17

Power Supply Harmonic Distortion

Better power factor = Lower harmonics because waveforms are cleaner

XP Power 18

Why is Harmonic Distortion a Problem?


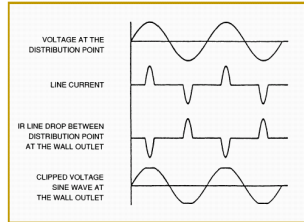


FIGURE 16
Waveforms illustrating the peak flattening effect that the narrow current pulses impose on the mains voltage

Harmonic Currents and Reactive Power

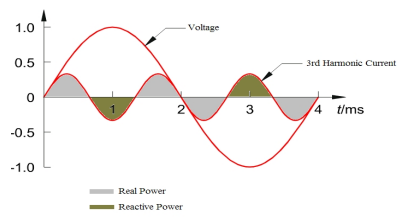

Main Effects of Low Power Factor

- Mains Voltage Distortion
- Oversizing of conductors
- Overheating of Neutral conductors
- Electromagnetic load failures
- Circuit Breakers Tripping
- Must take into account when working out efficiency