

1. Why have signal and control interfaces on power supplies?

• To monitor the condition of the input voltage
• To monitor the condition of the output voltage
• To monitor the internal temperature
• To control the power supply
• To adjust the output voltage / output current limitation


## 2. Differentiation between signal and control interfaces Signals The signals monitor the condition of the input voltage, output voltage, internal temperature via signal connections to control application, they have no influence to the function of the AC/DC or DC/DC converter. Control The control interface allows a change of parameters - output voltage, output current or ON / OFF. XP Power


### 3. Commonly used signal and control interfaces at PSU's

- AC OK / Power Fail Signal
- DC OK / Power Good Signal / PFD (Power Fail Detect Signal)
- System Reset Signal ( VME signal)
- Remote ON/OFF / Remote Control / Inhibit / Enable
- Output voltage adjustment
- Output current adjustment
- Output Marginate
- Power Sharing / Current Sharing


XP Power

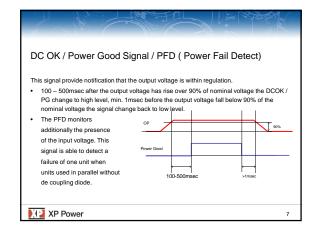
## AC OK / Power Fail Signal This signal indicate the condition of the input voltage. ACOK change from low to high after AC is switched on. The PF change to low level before the output voltage leave the tolerance range. This signal only detect if the input voltage is in the specified range. 1 = line voltage is selfiched on 2 = culput voltage within specified biserance 3 = culput voltage within specified biserance 5 = culput voltage within specified biserance 4 = line voltage fails or is switched off 5 = Fire Spring develops ower failure 6 = output voltage guits specified tolerance range XP Power




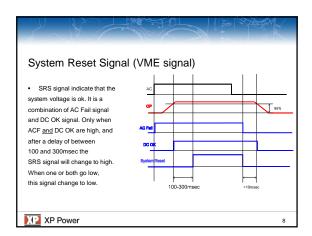


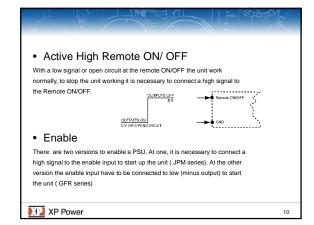
# Remote ON / OFF / Remote Control / Inhibit / Enable With the Remote ON/OFF signal it is possible to switch the output of a converter ON/OFF without touching the input voltage. The Remote ON/OFF function could be used for sequencing output voltages in systems multi outputs (e.g. LP / MP series). There are usually three types of Remote ON/OFF / Enable. • Active Low Remote ON/ OFF Through the connection of the Remote ON/OFF input with the output low the unit is switched off. Opening this connection, the unit start working.



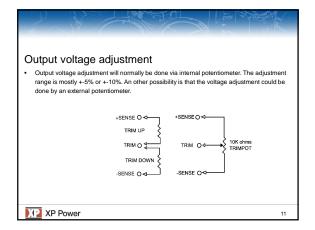

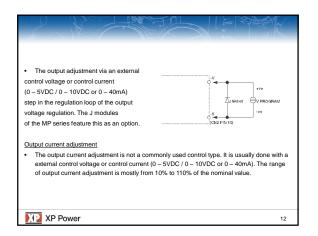

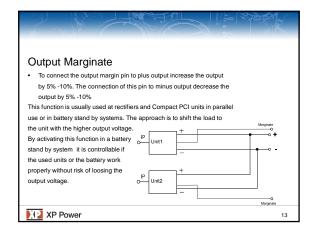

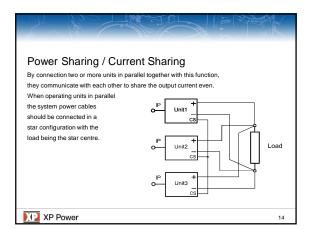

## 4. Which topologies are common for signal and control interfaces TL compatible signals: By TL circuits By standard transistors Open collector signals: Connected to the output Isolated from the output Volt free signals: Isolated signal created with opto coupler Isolated signal created with relays contacts

